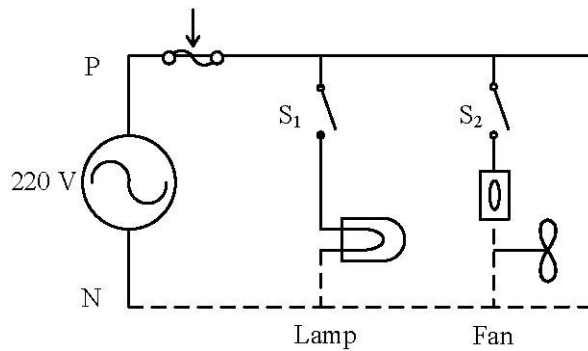


House Wiring Circuits in TinkerCAD


Objectives:

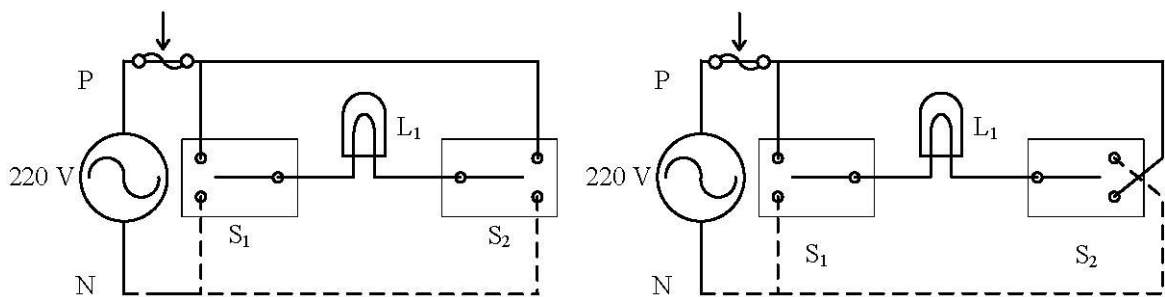1. To make a simple wiring circuit for two lamps
2. To make a staircase wiring/corridor wiring/godown wiring


Circuit



Wiring Circuit for a Lamp, Fan and Socket



Stair Case Wiring Circuit

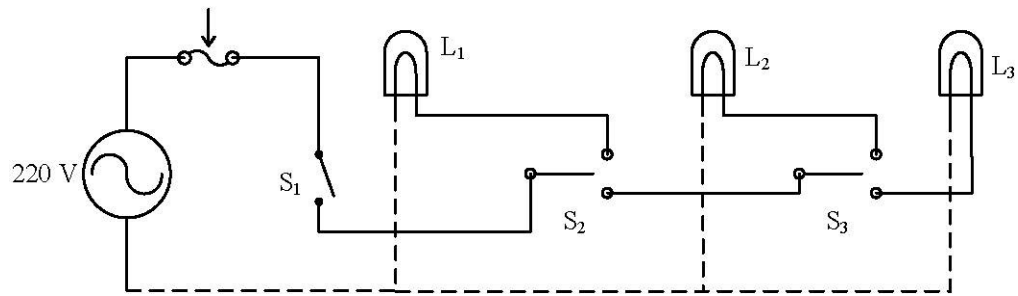

Corridor/Godown Wiring Circuit


Observation:

S. No	Parameter to be measured	Value Measured/ Calculated
1	Voltage Across L1	12V
2	Current drawn by L1	250 mA
3	Power Absorbed by L1	3W
4	Equivalent Resistance of L1	48Ω

Staircase Wiring Observation:

Switch 1	Switch 2	Lamp1 (XOR LOGIC)
OFF	OFF	OFF
ON	OFF	ON
OFF	ON	ON
ON	ON	OFF


Double Port Single Throw (DPST) Switch:

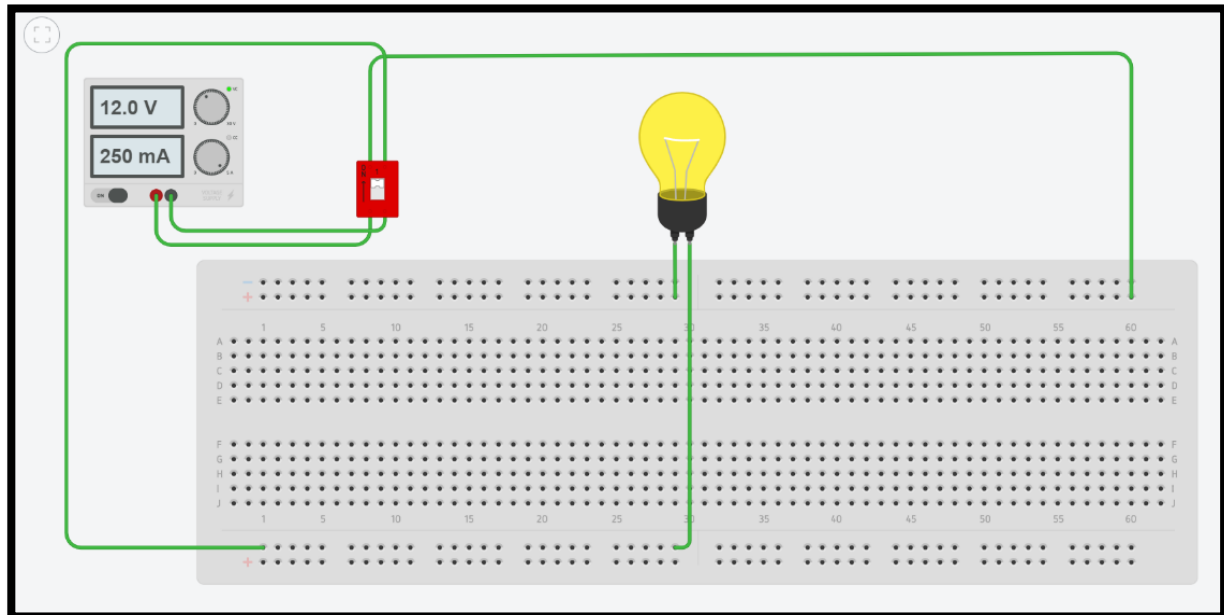

Calculation:

Voltage across $L1 = 12V$
Current drawn by $L1 = 250mA = 250 \times 10^{-3}A$
Power absorbed by $L1 = VI = 12 \times 250 \times 10^{-3}$
 $= 3000 \times 10^{-3}$
 $P_A = 3W$
Equivalent Resistance $= \frac{V}{I} = \frac{12 \times 10^3}{250}$
 $R_{L1} = 48\Omega$
Suitable fuse rating $= 2I = 500mA$

Staircase Wiring:

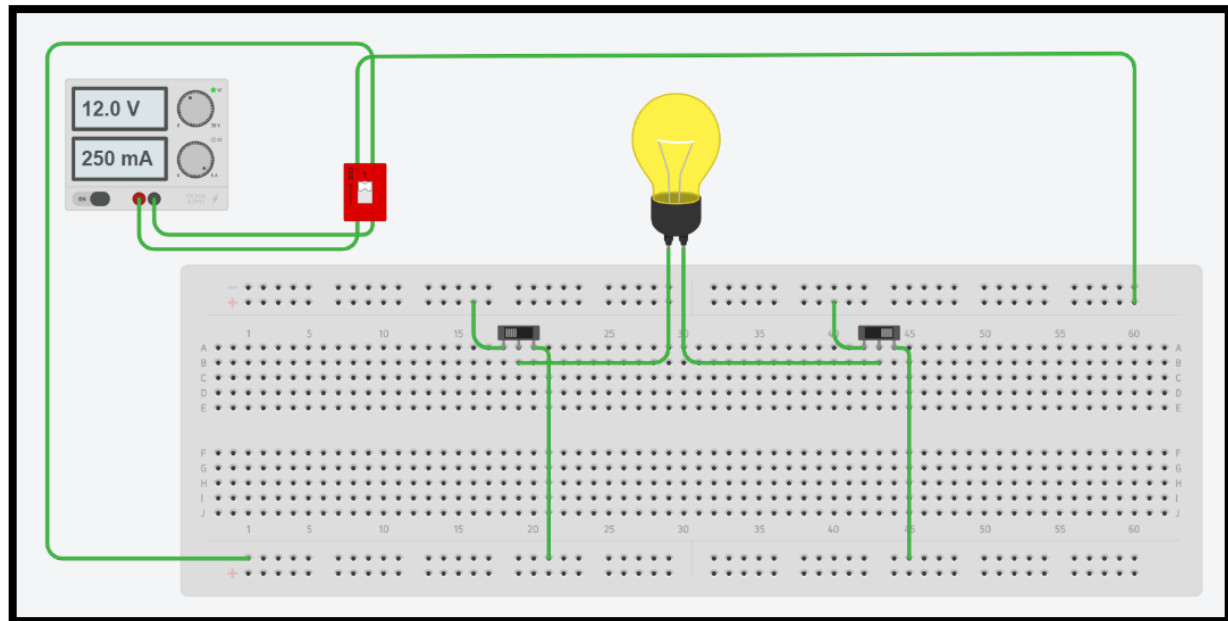

Godown Wiring:

