

## Transients in RC Circuits

### Objective:

To Study the transient phenomenon in series RC Circuit.


### Application:

1. RC circuit can be used to provide time delays. The warning blinkers usually found on road construction sites is an example. An electronic photoflash unit is another common example. *It exploits the ability of the capacitor to oppose any abrupt change in voltage*

### Simulation Tool:


LTSpice – transient analysis

### Switching Phenomenon in Circuits:

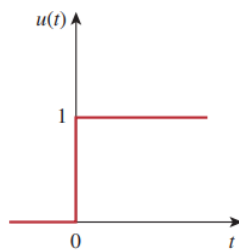


**Unit Step Signal** - Used to model a sudden change in dc voltage or switching  
In mathematical terms,
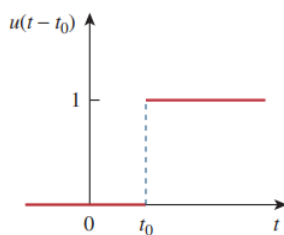
$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$



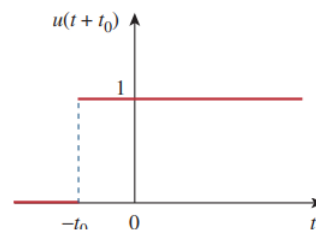
$$u(t - t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$




$$u(t + t_0) = \begin{cases} 0, & t < -t_0 \\ 1, & t > -t_0 \end{cases}$$


## Step Response of a RC Circuit

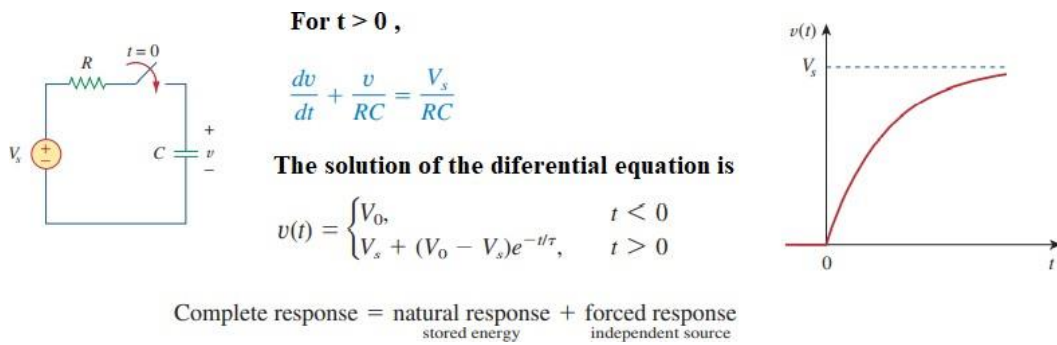

## Step Input – Modelled as Switch

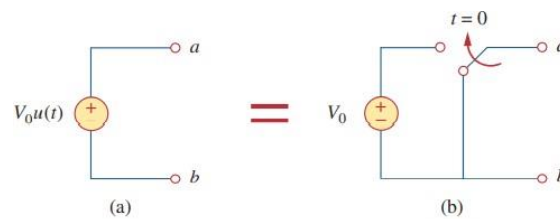

## Simulation Circuits:

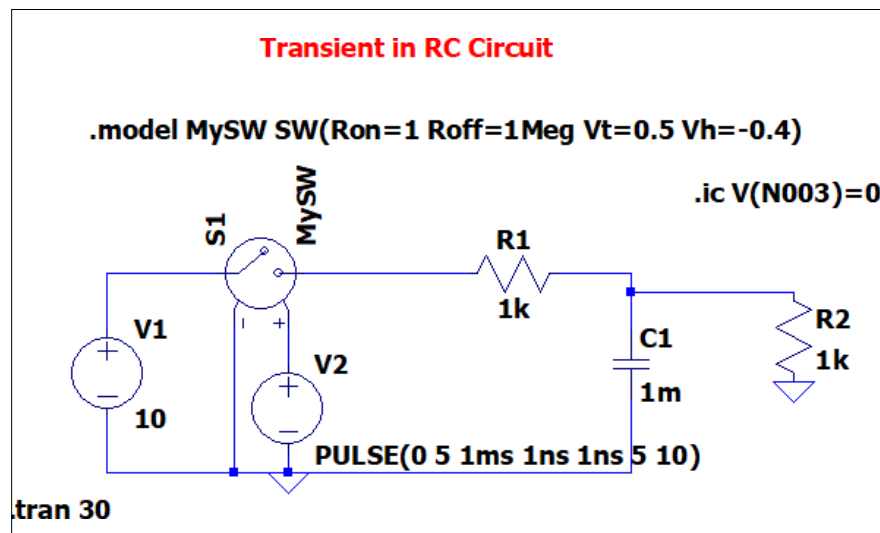


Observe the step response of both the circuits with input being the step voltage, and output is the voltage across the capacitor.


Ref: (Voltage Controlled Switches)

<https://www.analog.com/en/technical-articles/ltspiceiv-voltage-controlled-switches.html>


1)  $R1 = 500\Omega$ ,  $C1 = 5\mu$

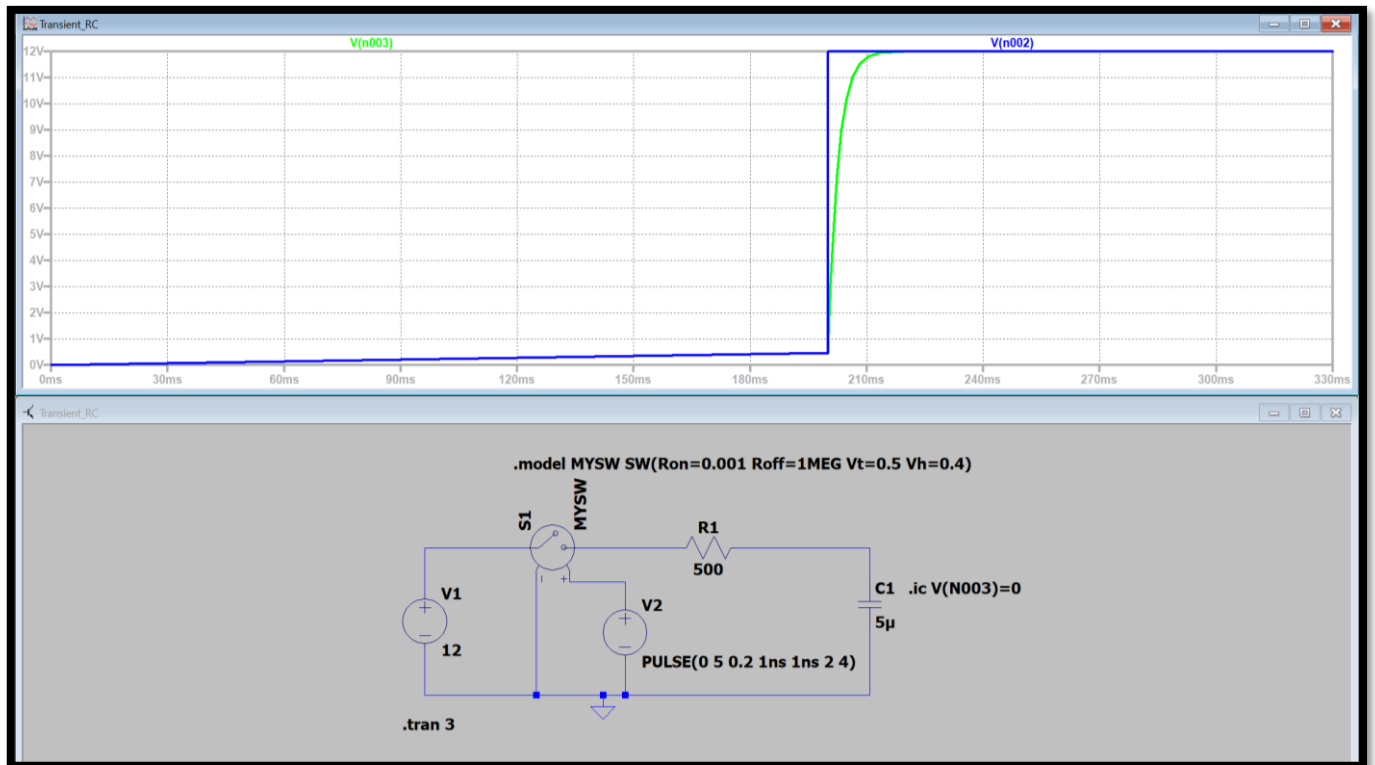

2)  $R1 = 1k\Omega$ ,  $C1 = 5\mu$

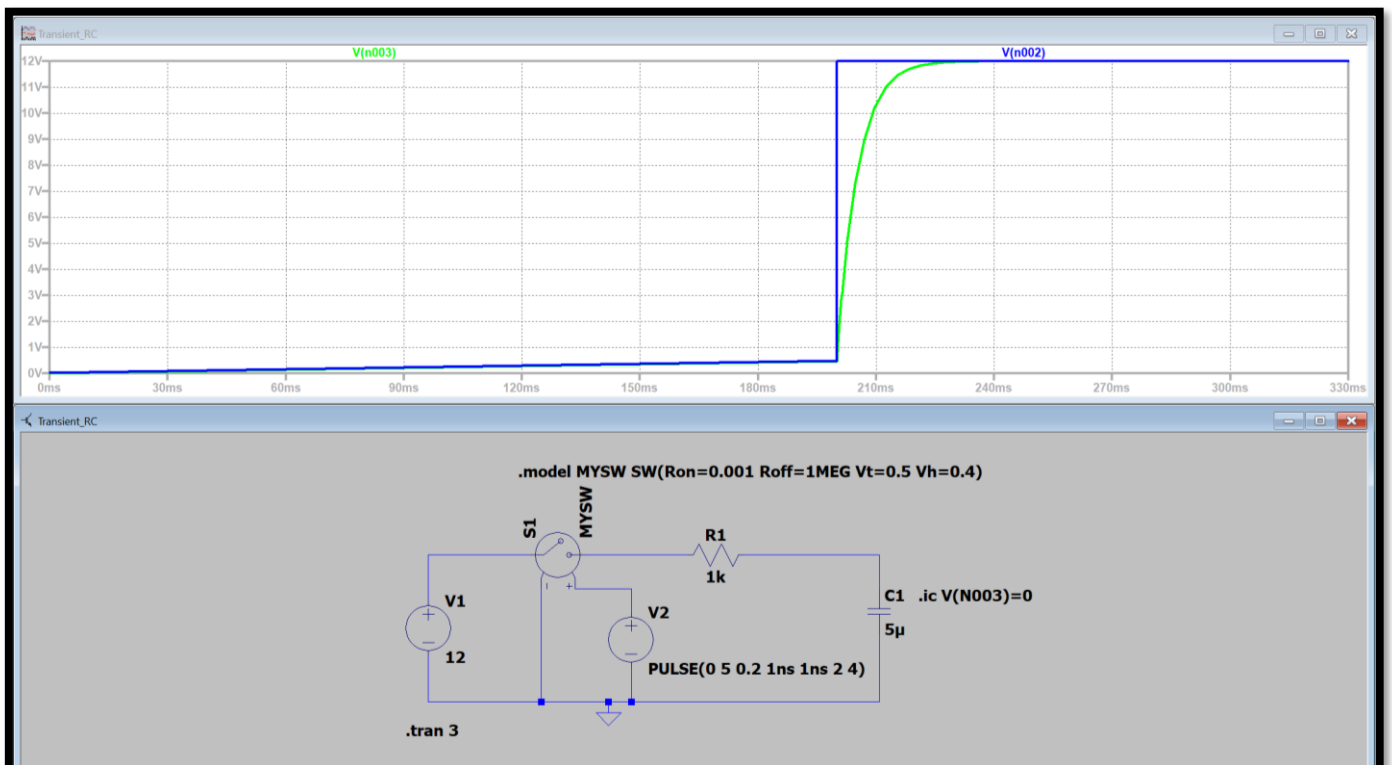

3)  $R1 = 10k\Omega$ ,  $C1 = 5\mu$

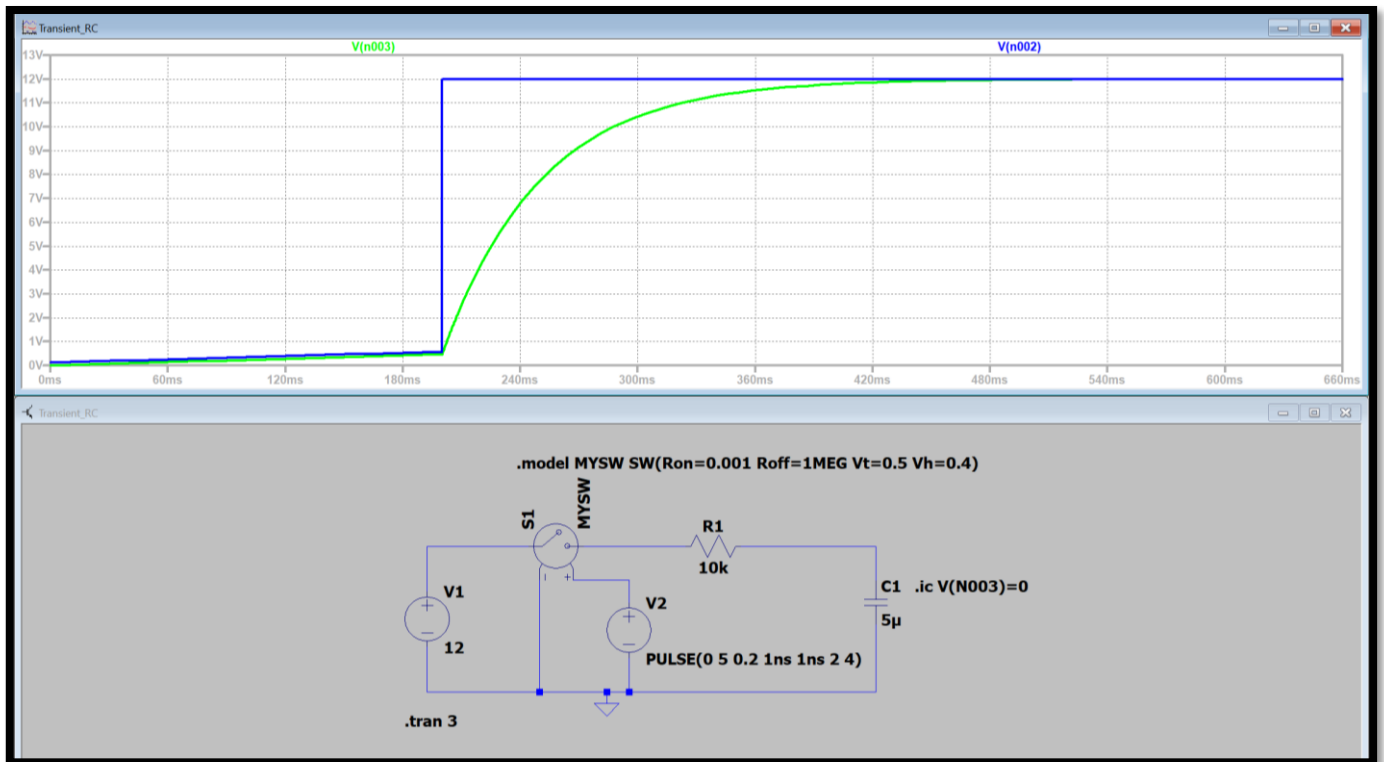

4)  $R1 = 1k\Omega$ ,  $C1 = 100$

