
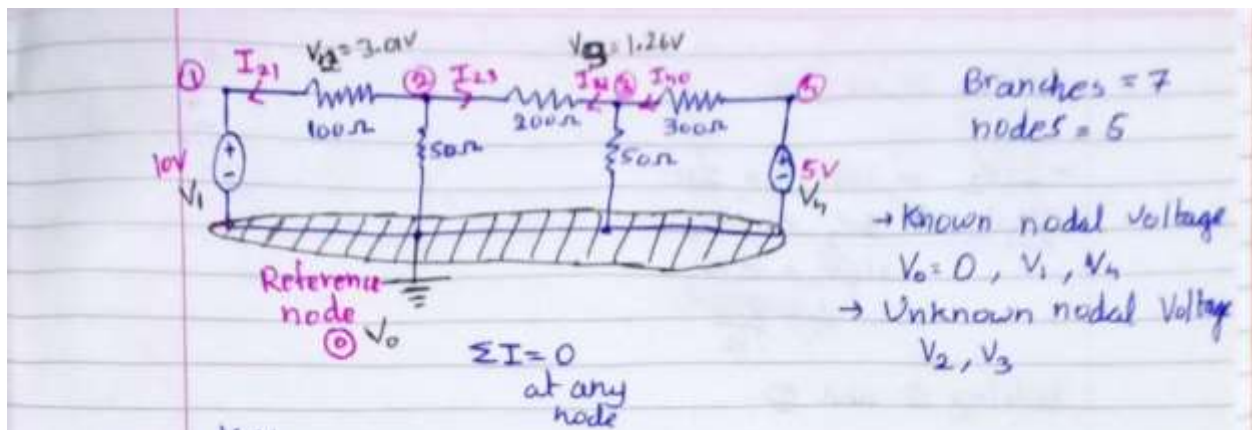


Verification of Kirchhoff's Current Law

Objectives:

1. To verify KCL and find the Nodal Voltages
2. To verify it on breadboard on www.tinkercad.com

Verification of KCL and Nodal Voltages

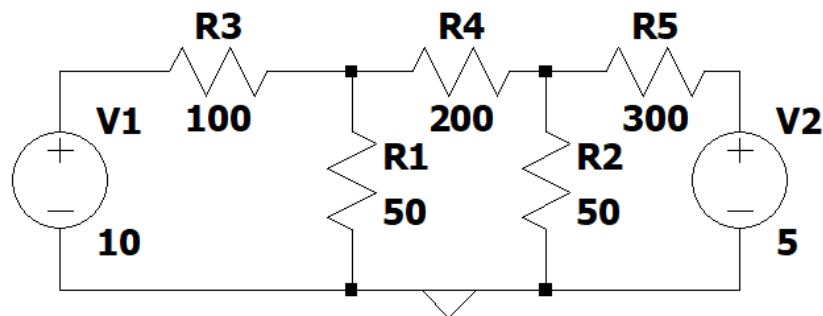

Observation:

S.No	Parameter to be measured	Value Measured with Units
1	V_2	3.01V
2	V_3	1.12V
3	I_{12} : Current through R_1	0.069A
4	I_{23} : Current through R_2	0.009A
5	I_{34} : Current through R_3	-0.0129A
6	I_{20} : Current through R_4	0.0602A
7	I_{30} : Current through R_5	0.0225A

Calculations:

• KCL
Node 2 $\sum I_{\text{entering node}} = \sum I_{\text{leaving node}}$

$$I_{02} = I_{21} + I_{23}$$
$$\Rightarrow \frac{0 - V_2}{50} = \frac{V_2 - V_1}{100} + \frac{V_2 - V_3}{200}$$
$$\Rightarrow -\frac{V_2}{50} = \frac{V_2 - 10}{100} + \frac{V_2 - V_3}{200}$$
$$\Rightarrow -4V_2 = 2V_2 - 20 + V_2 - V_3$$
$$\Rightarrow \boxed{7V_2 - V_3 = 20} \quad \text{--- (1)}$$

• KCL
Node 3 $\sum I_{\text{entering node}} = \sum I_{\text{leaving node}}$

$$I_{13} = I_{32} + I_{30}$$
$$\Rightarrow \frac{V_1 - V_3}{300} = \frac{V_3 - V_2}{200} + \frac{V_3 - V_0}{50}$$
$$\Rightarrow 2V_1 - 2V_3 = 3V_3 - 3V_2 + 12V_3 - 12V_0$$
$$\Rightarrow \boxed{17V_3 - 3V_2 = 10} \quad \text{--- (2)}$$

Solving ① and ②

$$-21V_2 + 119V_3 = 70$$

$$21V_2 - 3V_3 = 60$$

$$116V_3 = 130$$

$$V_3 = \frac{130}{116}$$

$$\Rightarrow V_3 = 1.1206V$$

$$\Rightarrow V_2 = 3.017V$$

$$I_{12} = \frac{10 - 3.01}{100\Omega} = 0.069A$$

$$I_{23} = \frac{3.01 - 1.126}{200\Omega} = 0.009A$$

$$I_{34} = \frac{1.126 - 5}{300\Omega} = -0.0129A$$



$$I_{20} = \frac{3.01 - 0}{50\Omega} = 0.0602A$$

$$I_{30} = \frac{1.126 - 0}{50\Omega} = 0.0225A$$

$$\begin{aligned} \text{Power supplied by } 10V &= V_1 \times I_{12} \\ &= 10 \times 0.069A = 0.69W \\ \text{Power dissipated in } 100\Omega &= V_{12} \times I_{12} \\ &= 6.99 \times 0.069 = 0.48W \end{aligned}$$

$$\begin{aligned} V_{12} &= V_{10} - V_{20} \\ &= 10 - 3.01 \\ &= 6.99V \end{aligned}$$

TinkercAD Circuit:

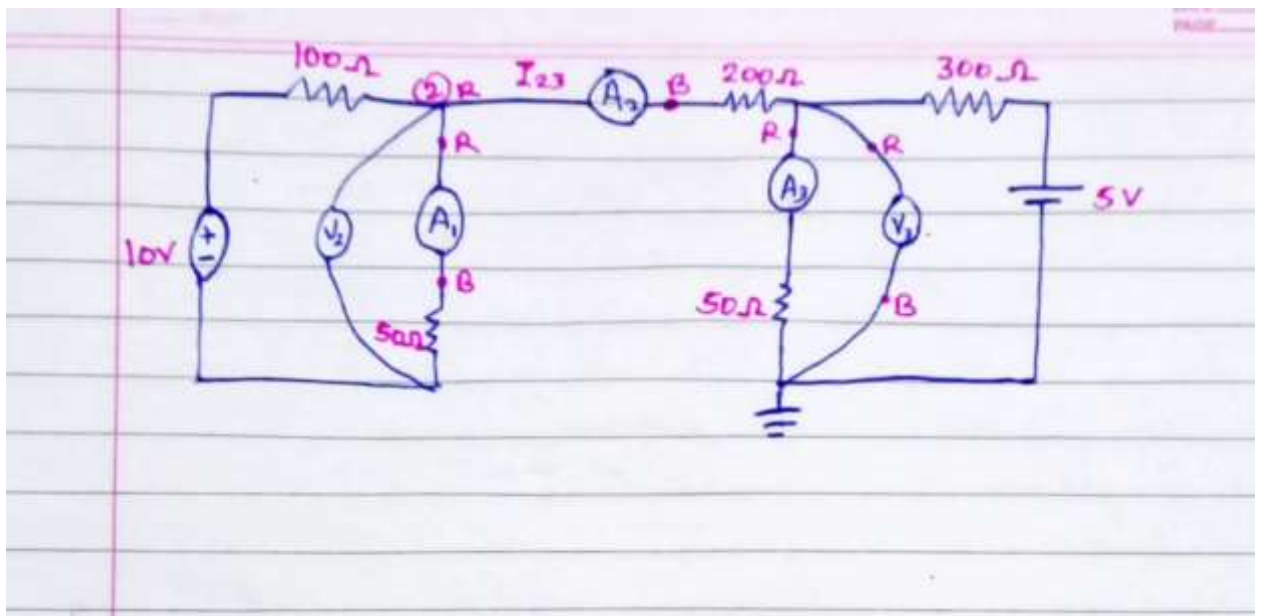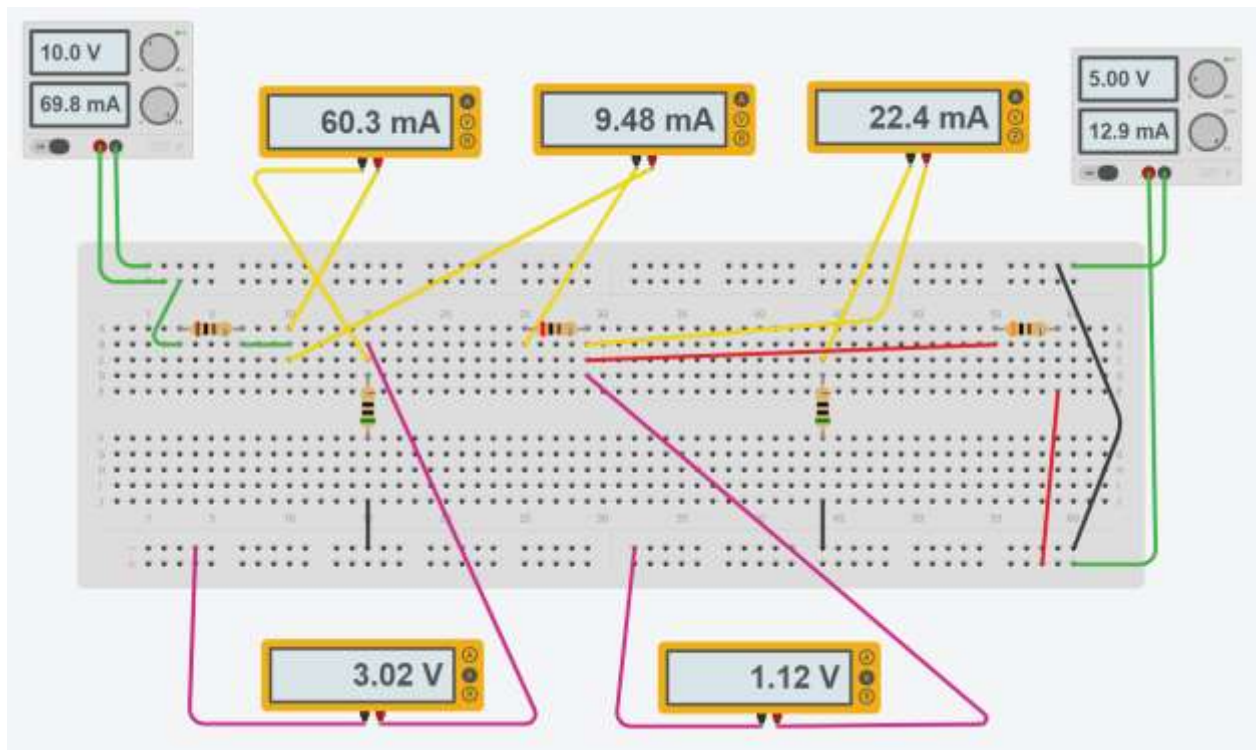

Shareable link: <https://www.tinkercad.com/things/9ctjWHqaSu7-stunning-densor/editel?sharecode=V3w64UNp21IDgh79C7hXV44ZR9-8KyT61ctrX9P6H7o>

To Do:

1. Verify KCL using the above measurements
2. Paste the Sharable link and Screenshot of Simulation done in TinkerCAD
3. Picture of the theoretical calculation done in your notebook